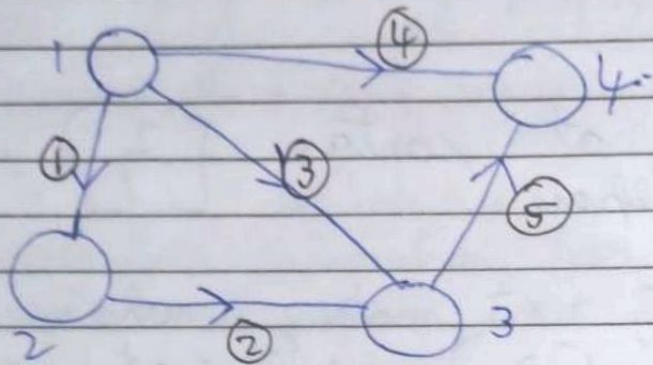


Lecture - 12

Graphs, Networks, Incidence Matrices

Let this be an circuit



$m = 5$ edges
 $n = 4$ nodes

* Incidence matrix

$$A = \begin{bmatrix} \text{Node 1} & \text{Node 2} & \text{Node 3} & \text{Node 4} \\ \begin{bmatrix} -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix} & \begin{matrix} \text{edge 1} \\ \text{edge 2} \\ \text{edge 3} \\ \text{edge 4} \\ \text{edge 5} \end{matrix} \end{bmatrix}$$

-1 indicates that the edge is going away from the node.

1 indicates that the edge is coming towards the node.

Edges 1, 2, 3 form a loop here.

Matrix only formed by edges 1, 2 and 3.

$$\begin{bmatrix} -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 1 & 0 \end{bmatrix}$$

This matrix has linearly dependent rows.
Row 1 + Row 2 = Row 3

* Nullspace

Solve $AX=0$

$$AX = \begin{bmatrix} x_2 - x_1 \\ x_3 - x_2 \\ x_3 - x_1 \\ x_4 - x_1 \\ x_4 - x_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$x = x_1, x_2, x_3, x_4$
Potentials at node

$\therefore x_2 - x_1, x_3 - x_2, \dots$ are all potential differences (PD)

For A to have nullspace, all PD's = 0.
i.e. All potentials must be equal.

Let all $x_1 = x_2 = x_3 = x_4 = 1$.

$$\therefore X = c \begin{bmatrix} 1 \\ 1 \\ 1 \\ 1 \end{bmatrix} \leftarrow \text{Null space}$$

$$\dim N(A) = 1$$

\therefore All PD's are zero, current won't flow through the circuit.

Now we ground the node x_4 .
i.e. $V_4 = 0$ ($x_4 = 0$)

\therefore The 4th column in A (column corresponding to x_4) becomes 0.

\therefore Rank of $A = 3 = r$

* Left Null Space, $N(A^T)$
 $A^T y = 0$

$$\dim N(A^T) = m - r = 5 - 3 = 2$$

$$A^T \text{ } n \times m \\ 4 \times 5$$

$$\begin{bmatrix} -1 & 0 & -1 & -1 & 0 \\ 1 & -1 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} y_1 \\ y_2 \\ y_3 \\ y_4 \\ y_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$e = Ax$$

$x_2 - x_1, \dots$
PD

$$y = C e$$

Ohm's law

$$A^T y = 0$$

Kirchoff's
current
law


Currents y_1, y_2, \dots, y_5
on edges

From $A^T y = 0$, we get

$$\begin{aligned} -y_1 - y_3 - y_4 &= 0 \\ y_1 - y_2 &= 0 \\ y_2 + y_3 - y_5 &= 0 \\ y_4 + y_5 &= 0 \end{aligned}$$

All these eqs when seen in the graph satisfy KCL i.e. summation of current at a node / Junction is 0.

For basis of $N(A^T)$

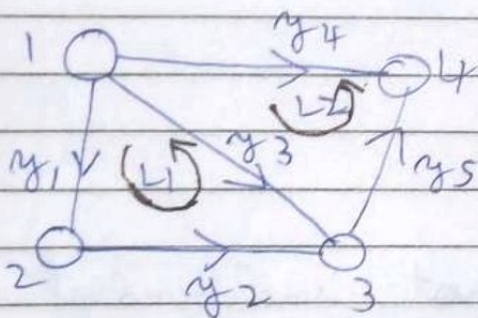

Send 1A current through loop 1 satisfying KCL

$$\begin{bmatrix} y_1 \\ y_2 \\ y_3 \\ y_4 \\ y_5 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \\ -1 \\ 0 \\ 0 \end{bmatrix} \leftarrow \text{Flow in opp direction}$$

Send 1 A current through loop 2
satisfying KCL

$$\begin{bmatrix} y_1 \\ y_2 \\ y_3 \\ y_4 \\ y_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 1 \\ -1 \\ 1 \end{bmatrix} \leftarrow \text{KCL direct}$$

If we consider loop 1234 $\boxed{1}$, $\boxed{2}$

$$\begin{bmatrix} y_1 \\ y_2 \\ y_3 \\ y_4 \\ y_5 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \\ 0 \\ -1 \\ 1 \end{bmatrix}$$

But this is not independent. It's a
combination of loop 1 and loop 2
solutions.

∴ Basis for $N(A^T)$ will only have
2 vectors

$$\left\{ \begin{bmatrix} 1 \\ 1 \\ -1 \\ 0 \\ 0 \end{bmatrix}, \begin{bmatrix} 0 \\ 0 \\ 1 \\ -1 \\ 1 \end{bmatrix} \right\}$$


* Row space of A

$$\dim(\text{row space of } A) = 3$$

i.e. No. of independent rows of A or no. of independent rows columns of A^T .

$$A^T = \begin{bmatrix} -1 & 0 & -1 & -1 & 0 \\ 1 & -1 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 1 & 1 \end{bmatrix}$$

First colm of A^T

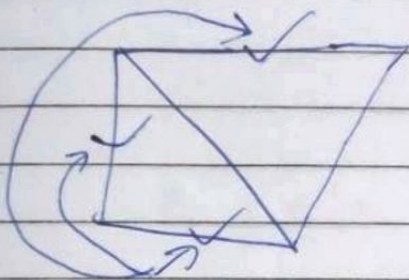

These are basis of row space of A

These ³ independent rows form a graph without a loop which is a tree.

$$\dim N(A^T) = m - r, \text{ rank} = r$$

$$\text{No of loops} = \text{No of edges} - \text{No of nodes} + 1$$

$$\therefore \boxed{\text{No of nodes} - \text{No of edges} + \text{No of loops} = 1}$$

This is Euler's formula which is true for any graph.


→ If we add current source to our circuit, $A^T y = 0$ changes to $A^T y = b$ where $b = \text{current source}$
 \downarrow PD
 $\therefore i = Ax$

But $y = Ce$
 $\therefore y = CAx$

But $A^T y = b$
 $\therefore \boxed{A^T CAx = b}$

Note: $A^T A$ is always a symmetric matrix

Q.

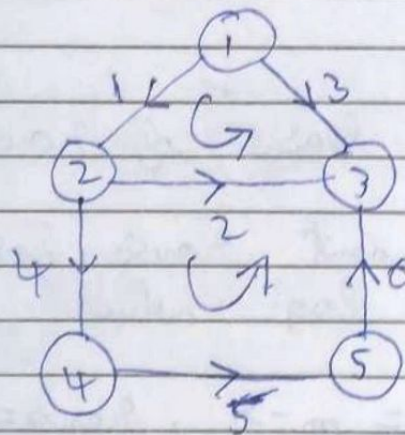

Find incidence matrix A

$N(A)$, $N(A^T)$

Trace $(A^T A)$

	Node1	Node2	Node3	Node4	Node5	
$A =$	-1	1	0	0	0	edge 1
	0	-1	1	0	0	edge 2
	-1	0	1	0	0	edge 3
	0	-1	0	1	0	edge 4
	0	0	0	-1	1	edge 5
	0	0	1	0	-1	edge 6

$$Ax = 0$$

This means that all potentials are equal.

$$\therefore N(A) = C \begin{bmatrix} 1 \\ 1 \\ 1 \\ 1 \\ 1 \\ 1 \end{bmatrix}$$

$$A^T y = 0$$

$$y = \begin{matrix} \swarrow \text{loop 1} & \swarrow \text{loop 2} \\ C_1 \begin{bmatrix} 1 \\ 1 \\ -1 \\ 0 \\ 0 \\ 0 \end{bmatrix} + C_2 \begin{bmatrix} 0 \\ -1 \\ 0 \\ 1 \\ 1 \\ 1 \end{bmatrix} \end{matrix}$$

- Trace($A^T A$) is sum of diagonal elements of $A^T A$.
- The diagonal entries of $A^T A$ are the magnitude squared of columns of A .
- Each entry of A is either $-1, 0$ or 1 .
∴ Square of entries will be either 0 or 1 .
- This equals to number of non-zero entries in each column.
- This tells us that Trace($A^T A$) is the sum of degrees of each node.

Degree of ① = 2

Degree of ② = 3

Degree of ③ = 3

Degree of ④ = 2

Degree of ⑤ = 2

Degree of ⑥ = 1

$$\therefore \text{Trace}(A^T A) = 2 + 3 + 3 + 2 + 2 + 1 = 13$$